



**B. TECH (CSE) - III SEM**

**UE23CS251A – DIGITAL DESIGN & COMPUTER  
ORGANIZATION**

**PROJECT DOCUMENTATION ON**

*Design and implement a circuit that counts the  
number of ones in a given input data.*

**SEC: C**

**Team Members:**

<b>S.No</b>	<b>SRN</b>	<b>NAME</b>
1.	PES1UG23CS157	Chaitanya M
2.	PES1UG23CS166	Chinmay Shivanand Muragod
3.	PES1UG23CS167	Chirag K M
4.	PES1UG23CS173	Darshith M S

**AUGUST – DECEMBER 2024**

**DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING**

**RR CAMPUS (MAIN CAMPUS)**

**BENGALURU – 560085, KARNATAKA**

## **TABLE OF CONTENTS**

Sl.No	TOPIC	PAGE No
1.	Idea for design	4
2.	Circuit Design	5
3.	Module code	6-7
4.	Commands to execute	8
5.	Output Screenshots	8
GITHUB LINK : <a href="https://github.com/ilb225112/DDCO_mini_proj">ilb225112/DDCO_mini_proj: 3rd Sem mini_proj for Digital Design and Computer Organization</a>		

HOW CAN WE COUNT NUMBER OF ONE'S IN A GIVEN DATA?



**HOW MANY 1's?**

## Basic idea:

The addition of Single binary bits in a row can also be understood in terms of the number of one's present:

for example,

Binary addition	SUM	No. of ones
0 + 0	0	Nil (0)
0 + 1	1	One (1)
1 + 1	10 -> 2	Two (2)
1 + 1 + 1	11 -> 3	Three (3)

. . .  
. . .  
. . .

0+0=0 indicates that **no** ones are present,

0+**1**=1 signifies that **only one** 1 is present, and

**1+1**=10 shows that there are **two one's** present.

**1+1+1**=11 shows that there are **3 one's** present and so on...

**So provided with any binary number adding all the individual bits would give us the Total no. of one's present in it.**


Note: The reason for choosing 7 bits

Initially on choosing 4 bits, the no. of bits required to represent output is 3, Because max number of 1's is 4->100 since 5,6,7 could also be represented using 3 bit we just chose 7 bit. Also, standard being 8 bits one of them would be sign bit, so we go for 7.

# Digital Circuit Design

- The circuit design for counting the number of ones in a 7-bit binary input is illustrated in the attached image.
- The image shows how the full adders are interconnected to facilitate the counting process. Use of 7-segment display is being done.
- For the seven-segment display K-map and connections are attached as a GitHub link at last of this file.
- It uses 4-Full adders. The continued part after full adders is for lab implementation

### Circuit Diagram:

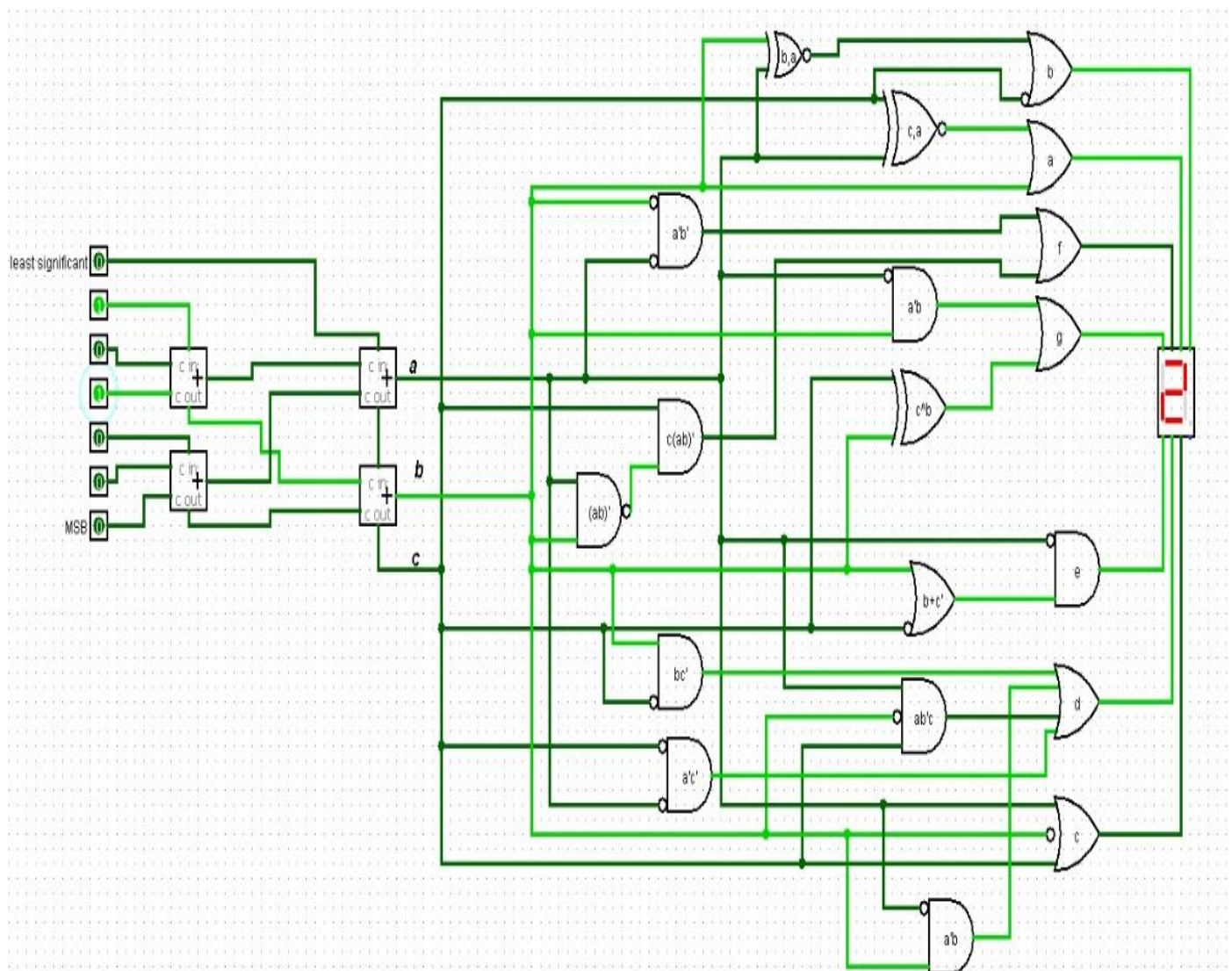

## Verilog Module (**norm1.v**)

### Full Adder Module (**fulladder**)

This module implements a single full adder, which takes three input bits and produces a sum and a carry-out bit.

```
module fulladder(  
    input wire a, b, cin,  
    output wire sum, cout  
);  
  
    assign sum = a ^ b ^ cin;  
    assign cout = (a & b) | (cin & (a ^ b));  
endmodule
```

### Sum Module (**output**)

This module utilizes multiple instances of the full adder to sum the bits of the input data and produce the output.

```
module sum(  
    input wire [6:0] inp,  
    output wire [2:0] op  
);  
  
    wire c1, c2, s1, s2, c3;  
  
    fulladder a1 (.a(inp[3]), .b(inp[2]), .cin(inp[1]), .sum(s1), .cout(c1));  
    fulladder a2 (.a(inp[6]), .b(inp[5]), .cin(inp[4]), .sum(s2), .cout(c2));  
    fulladder a3 (.a(s1), .b(s2), .cin(inp[0]), .sum(op[0]), .cout(c3));  
    fulladder a4 (.a(c1), .b(c2), .cin(c3), .sum(op[1]), .cout(op[2]));  
  
endmodule
```

## Testbench (**norm1\_tb.v**)

### Testbench Module:

The testbench module simulates various 7-bit input values to validate the functionality of the sum module.

```
`timescale 1ns/1ps

module testbench;
    reg [6:0] inp;
    wire [2:0] op;

    sum uut (
        .inp(inp),
        .op(op)
    );

    initial begin
        inp = 7'b0100100;
        #10;
        inp = 7'b0110101;
        #10;

        inp = 7'b1010000;
        #10;

        inp = 7'b1111111;
        #10;

        $finish;
    end

    initial begin
        $monitor("At time %t: inp = %b (%d), op = %d", $time, inp,inp, op);
    end

    initial begin
        $dumpfile("waveform.vcd");
        $dumpvars(0, testbench);
    end
endmodule
```


## Commands to execute:

```
Iverilog -o pr filename.v testbench.v  
vvp pr  
gtkwave waveform.vcd
```

## Compiler output:

```
C:\Windows\System32\cmd.e X + v  
Microsoft Windows [Version 10.0.22631.4317]  
(c) Microsoft Corporation. All rights reserved.  
  
C:\github\DDCO_mini_proj\4bit_basic_design>iverilog -o pr norm1.v norm1_tb.v  
  
C:\github\DDCO_mini_proj\4bit_basic_design>vvp pr  
VCD info: dumpfile waveform.vcd opened for output.  
At time          0: inp = 0100100 ( 36), op = 2  
At time        10000: inp = 0110101 ( 53), op = 4  
At time        20000: inp = 1010000 ( 80), op = 2  
At time        30000: inp = 1111111 (127), op = 7  
norm1_tb.v:26: $finish called at 40000 (1ps)
```

## GTKWave Simulation Results

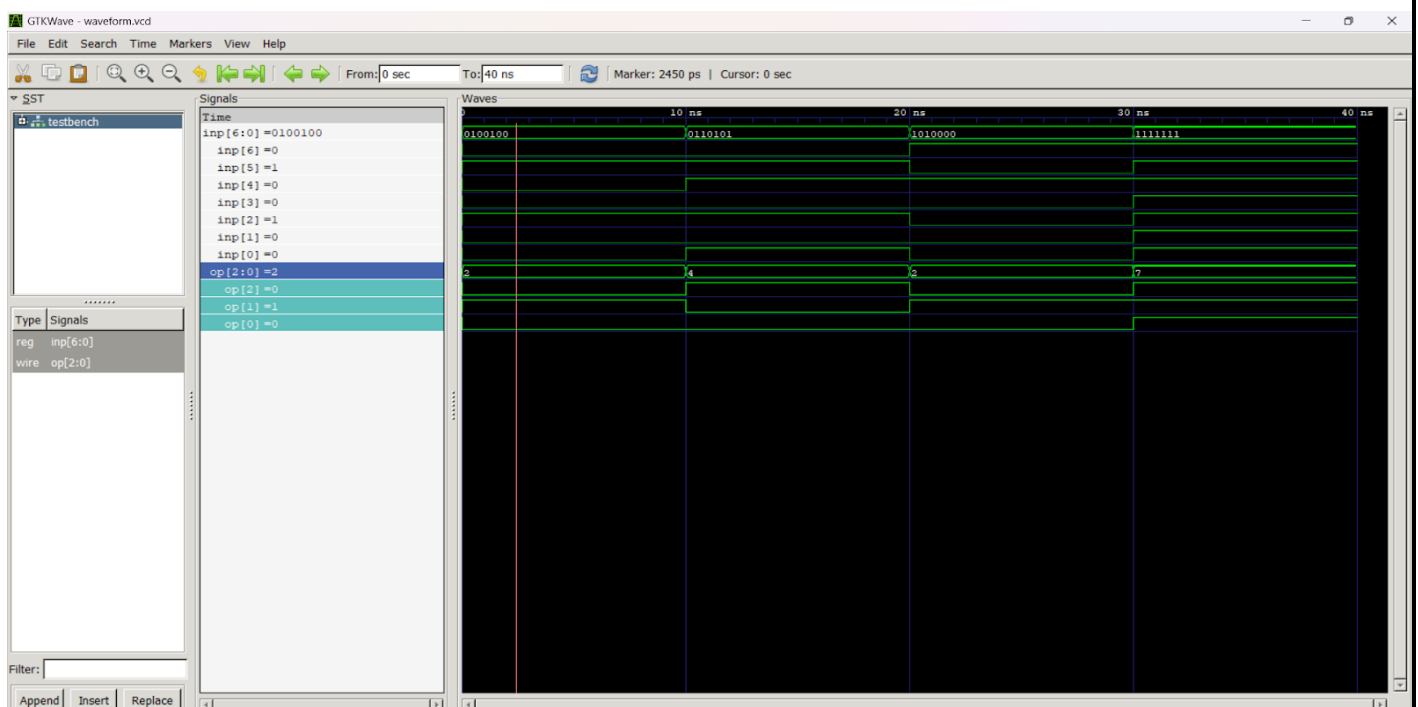



# THANK YOU



GITHUB LINK :

[ilb225112/DDCO\\_mini\\_proj](https://github.com/ilb225112/DDCO_mini_proj): 3rd Sem mini\_proj for Digital Design and Computer Organization